



CLASS : S.E. COMP

SUBJECT : DEL

EXPT. NO.: 7

DATE:

TITLE : Flip Flop Conversion

OBJECTIVE : To design and realize flip flop conversion



APPARATUS:

Digital-Board, IC 7476(Dual JK), 7408 (AND-gate), 7432 (OR-gate), D Flip flop

Theory:

JK Flip-Flop:

  
The JK Flip-Flop is basically a Gated SR Flip-Flop with the addition of clock input circuitry that prevents the illegal or invalid output that can occur when both input S equals logic level "1" and input R equals logic level "1". The symbol for a JK Flip-flop is similar to that of an SR Bi stable as seen in the previous tutorial except for the addition of a clock input.




The Truth Table for the JK Function

J	K	Q	Q	same as for the SR Latch
0	0	0	0	
0	0	1	1	
0	1	0	0	
0	1	1	0	
1	0	0	1	
1	0	1	1	
1	1	0	1	toggle action
1	1	1	0	

D Flip-Flop:

 


 It has only one input, D-input or data input. From the truth table it is clear that output Q_{n+1} at the end of clock pulse equals the input D_n before the clock pulse. It means input appears at the output at the end of the clock pulse. The output is delayed and hence the name is D Flip-flop.



Input D_n	Output Q_{n+1}
0	0
1	1

Pin Diagram

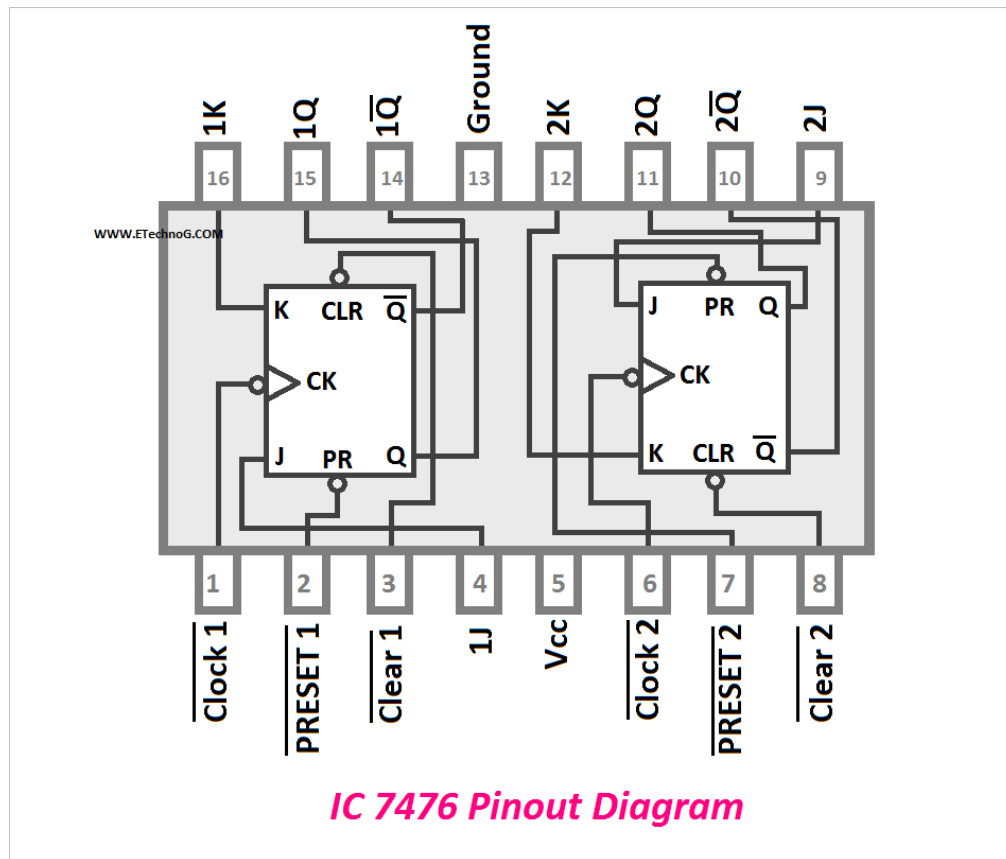

PROCEDURE:

1] Make connections as per the logic circuit for D flip flop to SR Flip flop and verify the truth table.

Conversion of D Flip Flop to SR Flip Flop

D is the actual input of the flip flop and S and R are the external inputs. Eight possible combinations are achieved from the external inputs S, R and Q_p. But, since the combination of S=1 and R=1 are invalid, the values of Q_{p+1} and D are considered as "don't cares". The logic diagram showing the conversion from D to SR, and the K-map for D in terms of S, R and Q_p are shown below.

D Flip Flop to S-R Flip Flop

Conversion Table


S-R Inputs		Outputs		D Input
S	R	Q _p	Q _{p+1}	
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	Invalid		Dont care
1	1	Invalid		Dont care

K-map

RQ _p	Q _p			
	00	01	11	10
0	0	1	0	0
1	1	1	X	X

$D = S + \bar{R}Q_n$

Logic Diagram

 

www.CircuitsToday.com

2] Make connections as per the logic circuit for JK flip flop to T Flip flop and verify the truth table.

JK Flip Flop to T Flip Flop

J and K are the actual inputs of the flip flop and T is taken as the external input for conversion. Four combinations are produced with T and Q_p. J and K are expressed in terms of T and Q_p. The conversion table, K-maps, and the logic diagram are given below.

J-K Flip Flop to T Flip Flop

Conversion Table

T Input	Outputs		J-K Inputs	
	Q _p	Q _{p+1}	J	K
0	0	0	0	X
0	1	1	X	0
1	0	1	1	X
1	1	0	X	1

K-maps


T	Q _p	
	0	1
0	0	X
1	1	X

$J = T$

T	Q _p	
	0	1
0	X	0
1	X	1

$K = T$

Logic Diagram

 

www.CircuitsToday.com



Logic Gates / MSI Device required for Implementation:

Sr.No.	Title	Name of the IC	Number of Gates required	IC Required
01	Conversion of D Flip Flop to SR Flip Flop			
02	JK Flip Flop to T Flip Flop			

Conclusion:

REFERENCE:

1. R.P.Jain "Modern Digital Electronics" TMH 4th Edition
2. D.Leach,Malvino,Saha,"Digital Principles and Applications",TMH

Subject teacher
Sign with Date

Remark