CLASS: S.E. COMPUTER SUBJECT: DEL

EXPT. NO.: 3 DATE:

TITLE : Design BCD Adder and Binary Adder using 4-bit Binary Adder

(IC 7483) and Realization of Binary Adder using IC 7483.

OBJECTIVE: To learn different types of adder

APPARATUS :

Digital Trainer Kit, IC 7483,7432 7408, GP-4Patch-Cords, + 5V Power

Supply required Logic gates if any.

THEORY :

Carry Save Adder:

Carry Propagation Adder:

The parallel adder is ripple carry type in which the carry output of each full adder stage is connected to the carry input of the next highest order stage.

Therefore, the sum and carry outputs of any stage cannot be produced until the carry occurs. This leads to a time delay in addition process.

This is known as Carry Propagation Delay.

- BCD Adder: It is a circuit that adds two BCD digits & produces a sum of digits also in BCD.
- ✓ Rules for BCD addition:

- 1. Add two numbers using rules of Binary addition.
- 2. If the 4 bit sum is greater than 9 or if carry is generated then the sum is invalid. To correct the sum add 0110 i.e. (6)10 to sum. If carry is generated from this addition add it to next higher order BCD digit.
- 3. If the 4 bit sum is less than 9 or equal to 9 then sum is in proper form.
- ✓ The BCD addition can be explained with the help of

Following 3 cases - CASE I: Sum \leq 9 & carry = 0.

Add BCD digits 3 & 4

1. 0011

+0100

0 1 1 1

Answer is valid BCD number = (7) BCD & so 0110 is not added.

CASE II: Sum > 9 & carry = 0.

Add BCD digits 6 & 5

1. 0110

+0101

1011

Invalid BCD (since sum > 9) so 0110 is to be added

Valid BCD result = (11) BCD

CASE III: Sum < = 9 & carry = 1.

Add BCD digits 9 & 9

Invalid BCD (since Carry = 1) so 0110 is to be added

2.
$$10010 \\ + 0110$$

$$11000$$

$$(1 8)BCD$$
Valid BCD result = (18) BCD



Design of BCD adder:

- 1. 4-bit binary adder is used for initial addition. i.e. binary addition of two 4-bit numbers. (with Cin = 0),
- 2. Logic circuit to sense if sum exceeds 9 or carry = 1, this digital circuit will produce high output otherwise its output will be zero.
- 3. One more 4-bit adder to add (0110)2 in the sum is greater than 9 or carry is

Truth Table: For design of combinational circuit for BCD adder to check invalid BCD

	OUTPUT				
S3	S2	S1 S0		Y	
0	0	0	0	0	
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	0	
0	1	0	0	0	
0	1	0	1	0	
0	1	1	0	0	
0	1	1	1	0	
1	0	0	0	0	
1	0	0	1	0	
1	0	1	0	1	
1	0	1	1	1	
1	1	0	0	1	
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	1	




K-map: -

For reduced Boolean expressions of output

S1S0								
S3S2		00	10	11	01			
	00	0	0	0	0			
	01	0	0	0	0			
	11	1	1	1	1			
	10	0	0	1	1			


Circuit diagram:

For invalid BCD detection

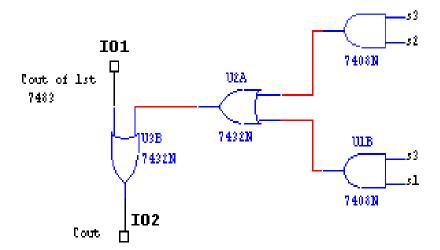




PIN DIAGRAM:

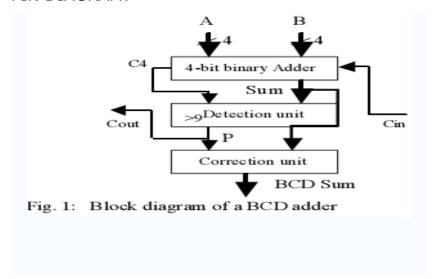

Circuit diagram for BCD adder:

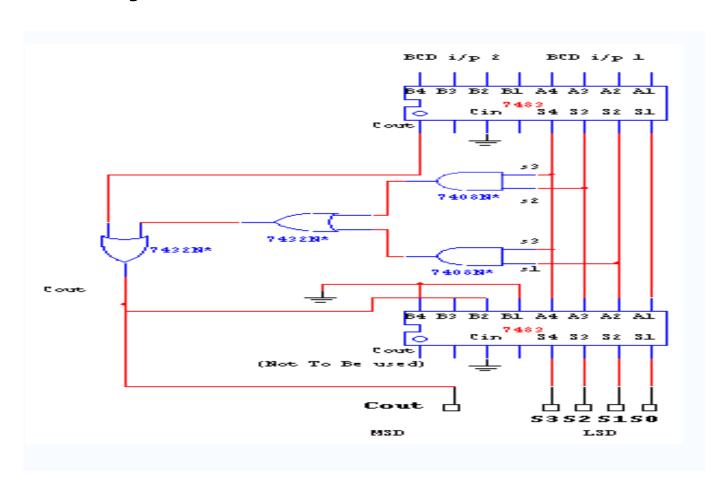



Observation Table of BCD adder:

INPUT						OUTPUT						
1st Operand			2nd Operand			MSD	LSD					
А3	A2	A1	A0	В3	В2	B1	во	Cout	S3	S2	S1	S0
(MSB)			(LSB)	(MSB)			(LSB)		(MSB)			(LSB)

OUTCOME:

Thus, we studied single bit BCD adder using 4 bit parallel binary adder / 4 bit full adder the observation table has been verified have been verified using IC 7483 & some logic gates.

REFERENCE:

- 1. R.P. Jain "Modern Digital Electronics" TMH 4th Edition
- 2. D.Leach, Malvino, Saha," Digital Principles and Applications", TMH